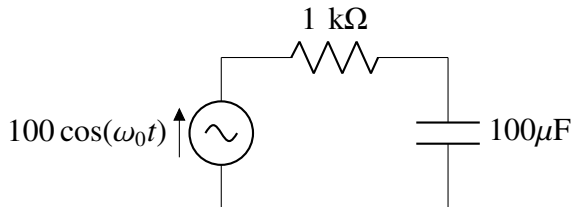


Gate Assignment

EE:1205 Signals and Systems
Indian Institute of Technology, Hyderabad

Kunal Thorawade
EE23BTECH11035

Question: In the circuit shown below, the amplitudes of the voltage across the resistor and the capacitor are equal. What is the value of the angular frequency ω_0 (in rad/s)? (Round off the answer to one decimal place.) (GATE BM 32 2023)



Solution:

Parameter	Value	Description
$v(t)$	$100 \cos(\omega_0 t)$	Input Voltage
R	$1 \text{ k}\Omega$	Resistance
C	$100 \mu\text{F}$	Capacitance
ω_0	?	Angular Frequency
$Z_R = R$	10^3	Impedance for resistor
$Z_C = \frac{1}{j\omega C}$	$\frac{10^4}{j\omega_0}$	Impedance for capacitor
$Z = R + \frac{1}{j\omega C}$	$10^3 + \frac{10^4}{j\omega_0}$	Total Impedance

TABLE 1
PARAMETER TABLE

$$R \xleftrightarrow{\mathcal{F}} R \quad (1)$$

$$C \xleftrightarrow{\mathcal{F}} \frac{1}{j\omega_0 C} \quad (2)$$

$$|V_R(\omega)| = |V_C(\omega)| \quad (3)$$

$$\Rightarrow |Z_R| = |Z_C| \quad (4)$$

$$10^3 = \frac{10^4}{\omega_0} \quad (5)$$

$$\therefore \omega_0 = 10.0 \quad (6)$$

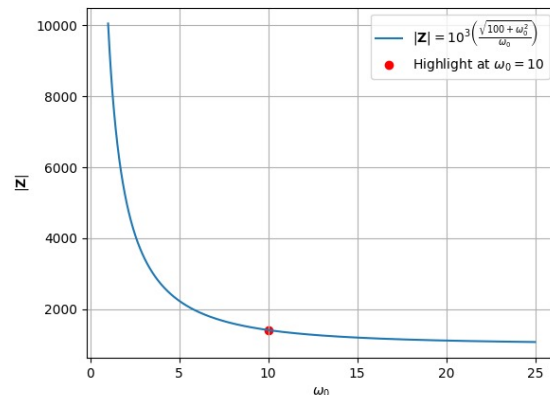
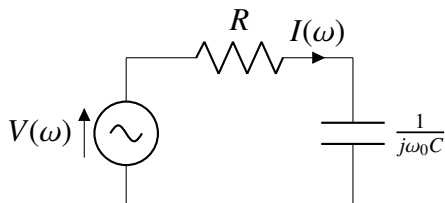


Fig. 1. Plot of $|Z| = 10^3 \left(\frac{\sqrt{100 + \omega_0^2}}{\omega_0} \right)$